

# GATE EC 2023

Mohiuddin

September 2023

1. In a given sequential circuit, initial states are  $Q_1 = 1$  and  $Q_2 = 0$ . For a clock frequency of 1 MHz, the frequency of signal  $Q_2$  in kHz, is (rounded off to the nearest integer)

